

Assignment-1

EE:1205 Signals and System
Indian Institute of Technology, Hyderabad

Prashant Maurya
EE23BTECH11218

I. QUESTION 12.7-15

A $100\mu\text{F}$ capacitor in series with a 40Ω resistance is connected to a 110V , 60Hz supply.

- (a) What is the maximum current in the circuit?
(b) What is the time lag between the current maximum and the voltage maximum?

Resistance of the resistor:

$$R = 40\Omega \quad (2)$$

Supply voltage:

$$V = 110\text{V} \quad (3)$$

(a) Frequency of oscillations:

$$\nu = 60\text{Hz} \quad (4)$$

Angular frequency:

$$\omega = 2\pi\nu = 2\pi \times 60 \quad (5)$$

Peak voltage:

$$V_0 = V\sqrt{2} = 110\sqrt{2}\text{V} \quad (6)$$

For an RC circuit, we have the relation for impedance as:

$$Z = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} \quad (7)$$

Maximum current is given as:

$$I_0 = \frac{V_0}{Z} \quad (8)$$

From (7), (8)

$$\Rightarrow I_0 = \frac{V_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \quad (9)$$

$$\Rightarrow I_0 = \frac{V_0}{\sqrt{40^2 + \frac{1}{(120\pi)^2 \times (10^{-4})^2}}} \quad (10)$$

$$\Rightarrow I_0 = 3.24 \quad (11)$$

II. SOLUTION

| Symbol | Value | Description |
|----------|---------------------------------------|-------------------|
| V | $110\text{V}, 60\text{Hz}$ | Voltage Supplied |
| R | 40Ω | Resistance |
| C | $100\mu\text{F}$ | Capacitance |
| ω | $2\pi\nu$ | Angular Frequency |
| ϕ | $\tan^{-1} \frac{1}{\omega CR}$ | Phase Angle |
| I_0 | $\frac{V_0}{Z}$ | Max Current |
| V_0 | $V\sqrt{2}$ | Peak Voltage |
| Z | $\sqrt{R^2 + \frac{1}{\omega^2 C^2}}$ | Impedance |
| $H(s)$ | $H(s) = \frac{V(s)}{I(s)}$ | Transfer Function |

TABLE 1: Given Parameters

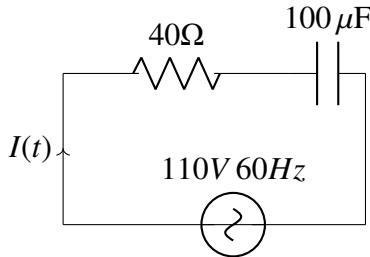


Fig. 1: RC Circuit

Capacitance of the capacitor:

$$C = 100\mu\text{F} = 100 \times 10^{-6} \quad (1)$$

(b) In a capacitor circuit, the voltage lags behind the current by a phase angle of ϕ . This angle is given by the relation :

$$\tan\phi = \frac{1}{\omega CR} \quad (12)$$

$$\Rightarrow \tan\phi = \frac{1}{120\pi \times 10^{-4} \times 40} \quad (13)$$

$$\Rightarrow \phi = \frac{33.56\pi}{180} \text{ rad} \quad (14)$$

$$\therefore \text{Time lag} = \frac{\phi}{\omega} \quad (15)$$

$$\Rightarrow \text{Time lag} = \frac{33.56\pi}{180 \times 120\pi} \quad (16)$$

$$\Rightarrow \text{Time lag} = 1.55 \text{ ms} \quad (17)$$

Hence, the time lag between maximum current and maximum voltage is 1.55 ms .

(c) Transfer Function is defined as:

$$H(s) = \frac{V(s)}{I(s)} \quad (18)$$

From (18)

$$H(s) = R + \frac{1}{sC} \quad (19)$$

$$\Rightarrow H(j\omega) = R + \frac{1}{j\omega C} \quad (20)$$

$$\Rightarrow |H(j\omega)| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} \quad (21)$$

$$\Rightarrow |H(j\omega)| = \sqrt{40^2 + \frac{1}{(120\pi)^2 \times (10^{-4})^2}} \quad (22)$$

$$\Rightarrow |H(s)| = 48 \quad (23)$$

$$\therefore I(s) = \frac{V(s)}{H(s)} \quad (24)$$

$$\Rightarrow I(s) = \frac{110}{48} \quad (25)$$

$$\Rightarrow I(s) = 2.29 \quad (26)$$

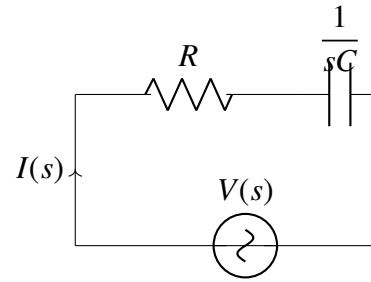


Fig. 2: RC Circuit

(d) Plot of Impedance vs Angular Frequency

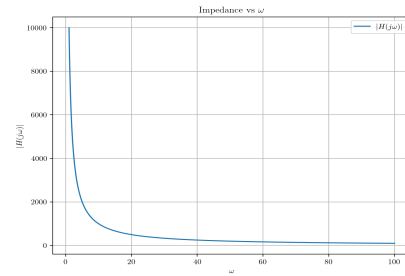


Fig. 3: Impedance vs ω

(e) Plot of Current vs Angular Frequency

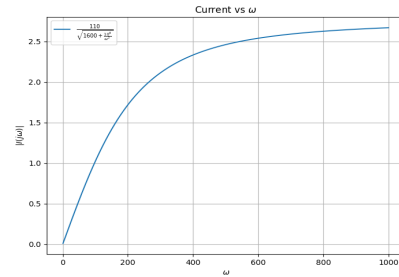


Fig. 4: Current vs ω